

LR CIRCUIT

Link to: [physicspages home page](#).

To leave a comment or report an error, please use the [auxiliary blog](#).

References: Griffiths, David J. (2007), Introduction to Electrodynamics, 3rd Edition; Pearson Education - Problem 7.29.

Suppose we have a circuit consisting of a battery delivering a voltage \mathcal{E}_0 , an inductor L and a resistor R , all in series. If the circuit has been connected long enough to stabilize, suppose we then throw a switch that bypasses the battery and isolates L and R in their own loop. The inductor will then produce some back emf that opposes the drop in current, in the amount $\mathcal{E} = -L\dot{I}$. Since this is now the only source of emf in the circuit, it must equal the voltage drop across the resistor, so

$$(1) \quad -L\dot{I} = IR$$

$$(2) \quad \dot{I} = -\frac{R}{L}I$$

$$(3) \quad I(t) = I_0 e^{-Rt/L} = \frac{\mathcal{E}_0}{R} e^{-Rt/L}$$

where I_0 is the initial current, which is $I_0 = \mathcal{E}_0/R$.

The total energy delivered to the resistor by the inductor is

$$(4) \quad W = R \int_0^\infty I^2(t) dt = I_0^2 R \int_0^\infty e^{-2Rt/L} dt = \frac{1}{2} L I_0^2$$

From the energy formula for an inductor, this is equal to the initial energy in the inductor's magnetic field.

$$(5) \quad W = \frac{1}{2} L \left(\frac{\mathcal{E}_0}{R} \right)^2$$